

## D-FF with input of AND gate

Block diagram:

 


Figure 1: Block diagram

Verilog code:

```
module Dff_with_andGate(  
    input clk,  
    input reset,  
    input a,  
    input b,  
    output reg q  
);  
  
    always @(posedge clk) begin  
        if (reset) begin  
            q <= 1'b0;  
        end  
        else begin  
            q <= a&b;  
        end  
    end  
endmodule
```

Schematics:

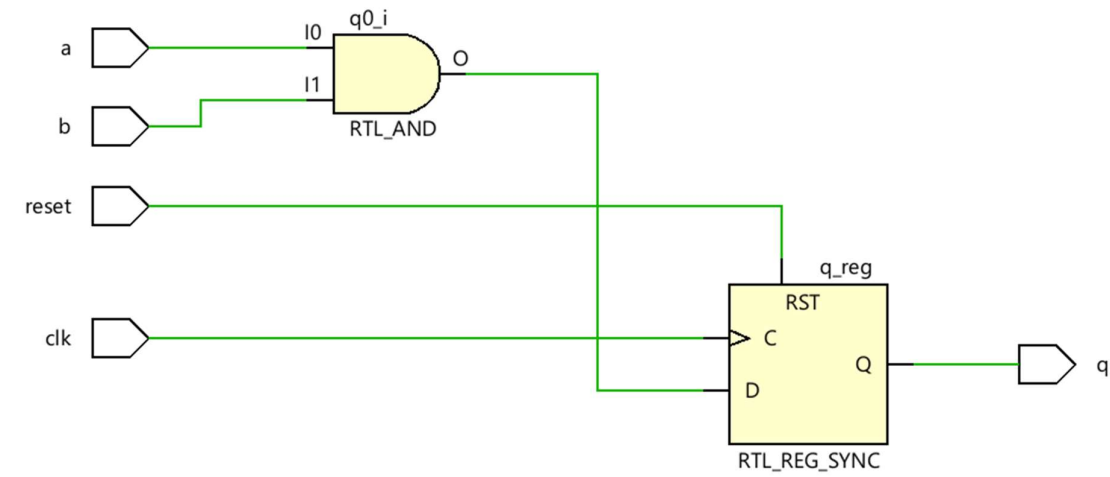


Figure 2: RTL Schematic

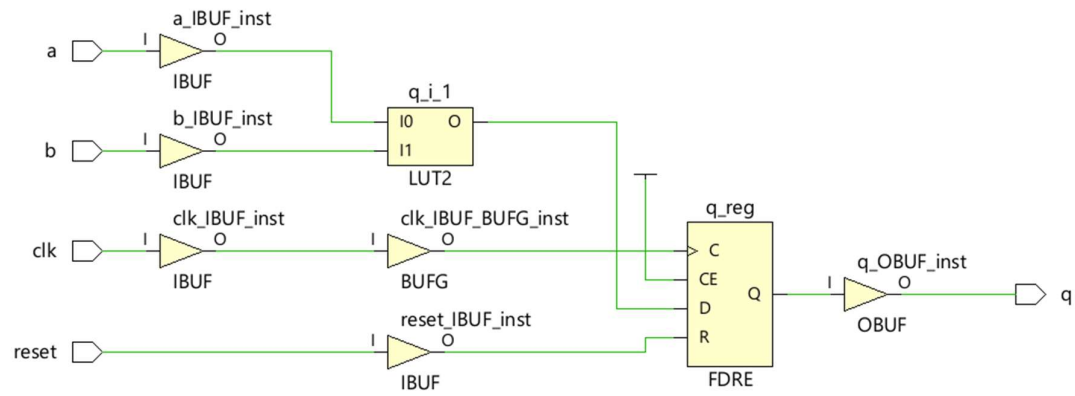


Figure 3: Synthesized Schematic

LUT:

Cell Properties		
q_i_1		
I1	I0	O=I0 ...
0	0	0
0	1	0
1	0	0
1	1	1

Figure 4: LUT2

Testbench code:

```
module Dff_with_andGate_tb;
```

```
reg clk;
```

```
reg reset;
```

```
reg a;
```

```
reg b;
```

```
wire q;
```

```
Dff_with_andGate a1(.clk(clk),.reset(reset),.a(a),.b(b),.q(q));
```

```
always #5 clk = ~clk;
```

```
initial begin
```

```
clk=0; reset=1; a=0; b=0;
```

```
#10;
```

```
reset=0;
```

```
#10; a=0; b=0;
```

```
#10; a=0; b=1;
```

```
#10; a=1; b=0;
```

```
#10; a=1; b=1;
```

```
#10; reset=1;
```

```
#10;
```

```
$finish;
```

```
end
```

```
initial begin
```

```
$monitor("Time=%0t | clk=%b | reset=%b | a=%b | b=%b | q=%b", $time, clk, reset, a, b, q);
```

```
end
```

```
endmodule
```

Timing diagram:

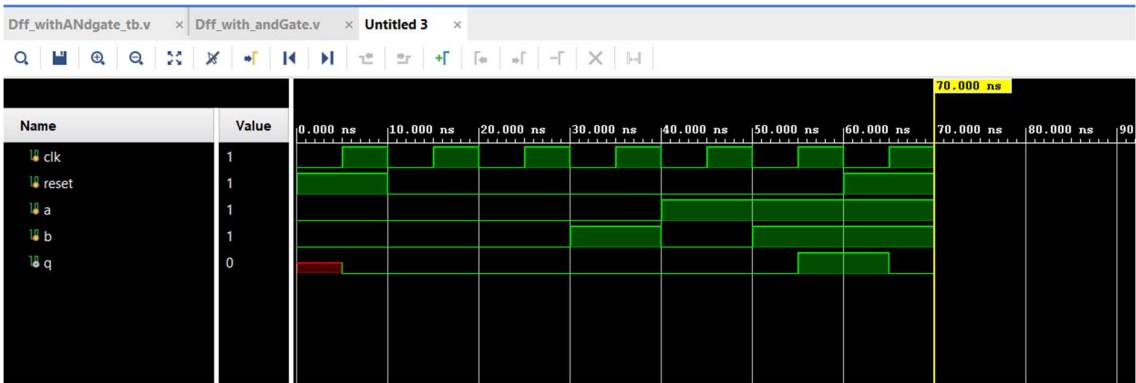


Figure 5: Timing diagram