

Distributed BRAM (256 width x 32 depth)

Distributed BRAM: Implemented using LUT's

As we have 256 various locations to be stored, therefore the address width is $\log_2(256)=8$ and the I/O lines are of 32 bit each. For distributed BRAM asynchronous read is the key part.

Verilog code:

```
module distributed_BRAM(  
    input clk,  
    input we,  
    input [7:0] addr,  
    input [31:0] din,  
    output [31:0] dout  
);  
    (* ram_type="distributed" *)  
    reg [31:0] mem [0:255];  
    always @(posedge clk) begin  
        if (we) begin  
            mem[addr]<=din;  
        end  
        end  
        assign dout = mem[addr];  
endmodule
```

Schematics:

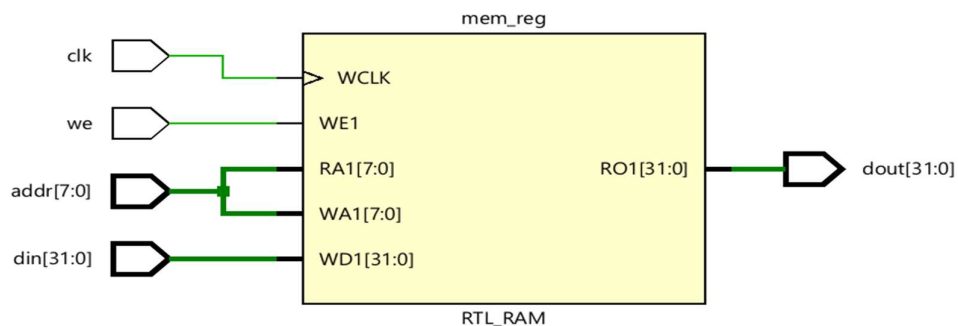


Figure 1: RTL Schematic

 


Figure 2: Synthesized Schematic

Above schematic the design utilizes block RAM256X1S, which is implemented using the LUT resources. Hence distributed BRAM is properly implemented.

Logic tables:

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	128	0	0	53200	0.24
LUT as Logic	0	0	0	53200	0.00
LUT as Memory	128	0	0	17400	0.74
LUT as Distributed RAM	128	0			
LUT as Shift Register	0	0			
Slice Registers	0	0	0	106400	0.00
Register as Flip Flop	0	0	0	106400	0.00
Register as Latch	0	0	0	106400	0.00
F7 Muxes	64	0	0	26600	0.24
F8 Muxes	32	0	0	13300	0.24

Figure 3: Slice logic table

2. Memory

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

Figure 4: Memory table